

Digital Systems Design and Laboratory

[Lab 2. Pipelined Multiplier]

TA: Sheng-Ya Lin

CSIE Department

National Taiwan University

Outline

- ❑ **Multiplier**
- ❑ Pipeline
- ❑ Fast Multiplier
- ❑ Assignment
- ❑ Appendix

Definition

❑ Unsigned multiplier


- Multiplicand \times Multiplier = Product
- Signed multipliers will not be covered in Lab 2

$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 \end{array} \\
 \begin{array}{l}
 \text{AB}_i \text{ called a "partial product"} \longrightarrow \begin{array}{cccc} A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \end{array} \\
 \begin{array}{cccc} A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \end{array} \\
 \begin{array}{cccc} A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \end{array} \\
 + \begin{array}{cccc} A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \end{array} \\
 \hline
 \end{array}
 \end{array}$$

Multiplying N-bit number by M-bit number gives (N+M)-bit result

Metrics

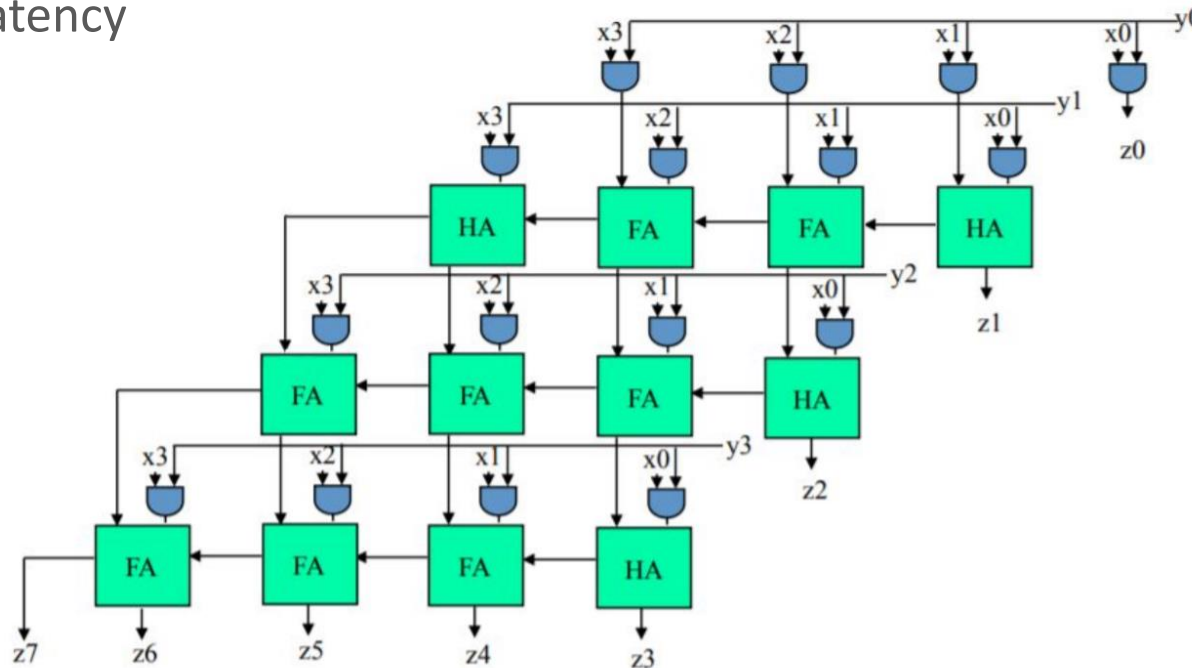- ❑ For an n -bit \times n -bit multiplier
- ❑ Latency (longest propagation delay)
 - $\approx 2n * \text{delay}(\text{FA})$
- ❑ Throughput (operations per second)
 - $\approx 1 / \text{Latency}$





Outline

- ❑ Multiplier
- ❑ **Pipeline**
- ❑ Fast Multiplier
- ❑ Assignment
- ❑ Appendix


How to Increase Throughput?

 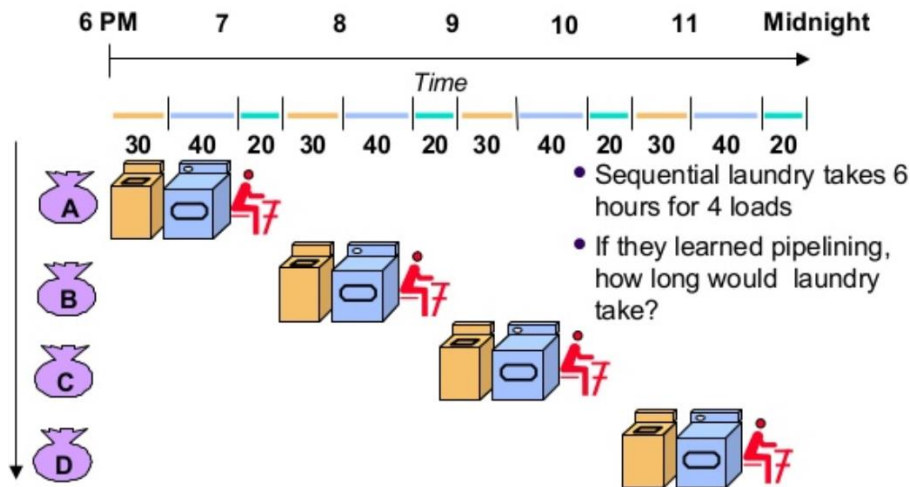- ❑ Cut the circuit into different stages
- ❑ Do different tasks in each stage at the same time
- ❑ Does the latency change? How about the throughput?



Pipelined Multiplier

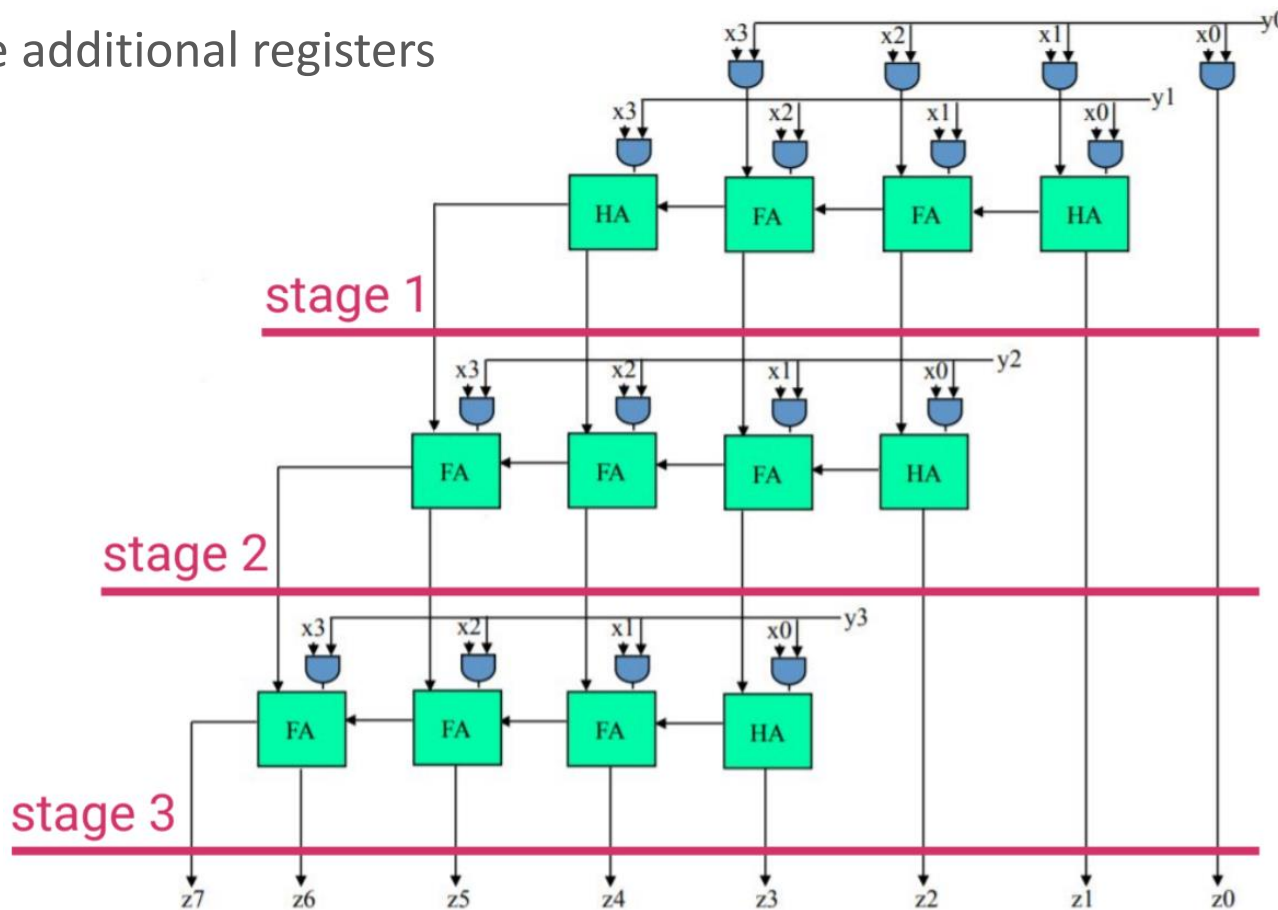- ❑ Add registers at the end of each stage to keep states
- ❑ $x[3:0]$ and $y[3:0]$ should also be kept in each stage
 - Use additional registers



Outline

- ❑ Multiplier
- ❑ Pipeline
- ❑ **Fast Multiplier**
- ❑ Assignment
- ❑ Appendix


Popular Techniques

- ☐ Carry-save adder
- ☐ Wallace tree
- ☐ High-radix
- ☐ And more ...

A Hierarchical Design

		$a_7 \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0$ $b_7 \ b_6 \ b_5 \ b_4 \ b_3 \ b_2 \ b_1 \ b_0$							
<div> $p_{ij} = a_i b_j$ </div>	L	$p_{70} \ p_{60} \ p_{50} \ p_{40} \ p_{30} \ p_{20} \ p_{10} \ p_{00}$							
	1	$p_{71} \ p_{61} \ p_{51} \ p_{41} \ p_{31} \ p_{21} \ p_{11} \ p_{01}$							
	L	$p_{72} \ p_{62} \ p_{52} \ p_{42} \ p_{32} \ p_{22} \ p_{12} \ p_{02}$							
	1	$p_{73} \ p_{63} \ p_{53} \ p_{43} \ p_{33} \ p_{23} \ p_{13} \ p_{03}$							
	L	$p_{74} \ p_{64} \ p_{54} \ p_{44} \ p_{34} \ p_{24} \ p_{14} \ p_{04}$							
	1	$p_{75} \ p_{65} \ p_{55} \ p_{45} \ p_{35} \ p_{25} \ p_{15} \ p_{05}$							
	L	$p_{76} \ p_{66} \ p_{56} \ p_{46} \ p_{36} \ p_{26} \ p_{16} \ p_{06}$							
	1	$p_{77} \ p_{67} \ p_{57} \ p_{47} \ p_{37} \ p_{27} \ p_{17} \ p_{07}$							

A Hierarchical Design

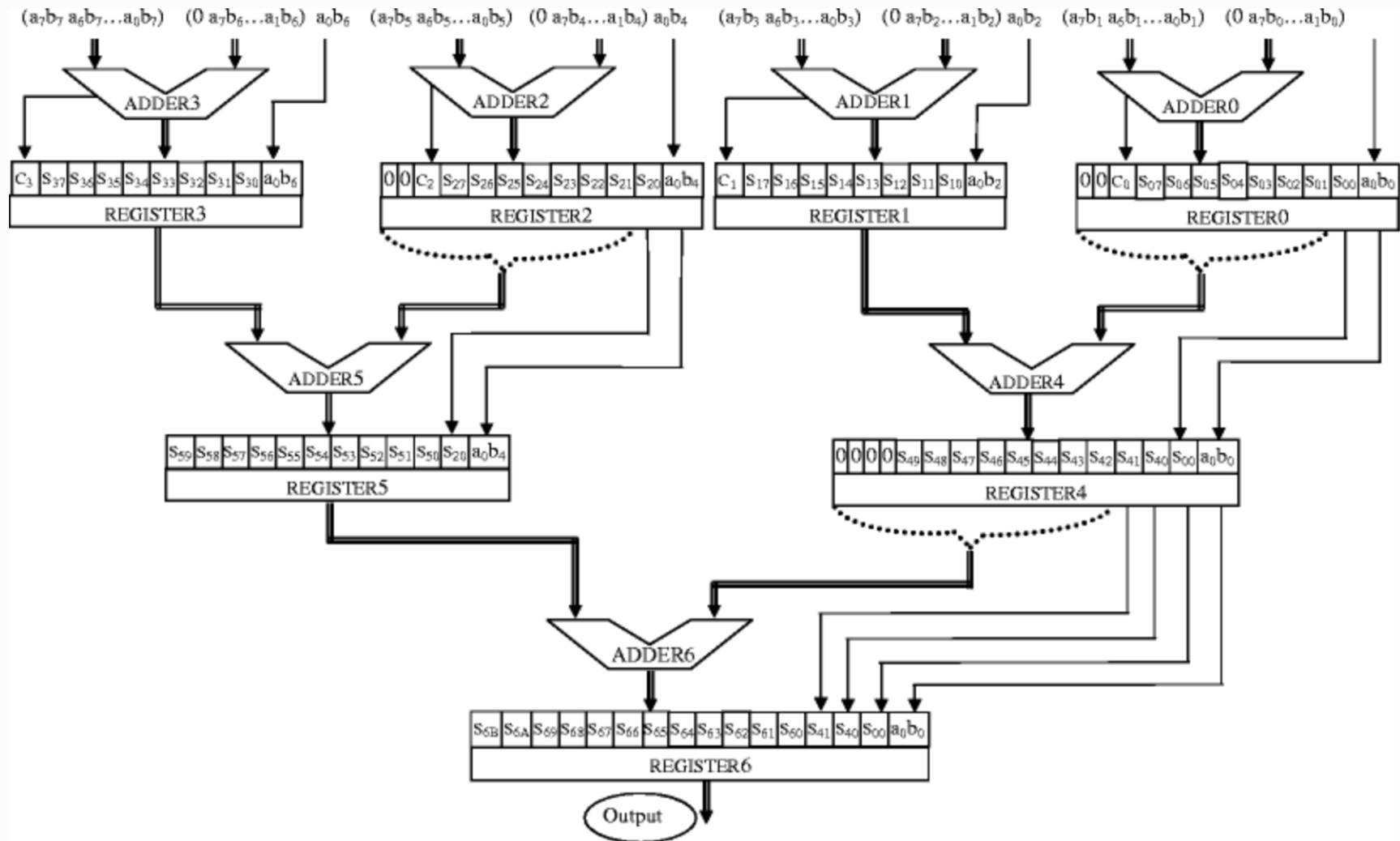

Outline

- ❑ Multiplier
- ❑ Pipeline
- ❑ Fast Multiplier
- ❑ **Assignment**
- ❑ Appendix

Execution

- ❑ Download the sample code

- ❑ Compile

 - `> iverilog -o lab2.vvp lab2.v`

- ❑ Simulate

 - `> vvp lab2.vvp`

 - Generates `lab2.vcd`

- ❑ View waveform

 - `> gtkwave lab2.vcd lab2.sav`

Requirements (1/2)

- ❑ Replace **<index>** in **lab2.v** with proper indexes
 - Leave the rest of the code unchanged
- ❑ Show your source code
- ❑ Show the waveform with the settings in **lab2.sav**
- ❑ What is the latency?
 - Worst case waiting time from the input becomes steady to the register of the last stage refreshes
 - Use tick as time unit

Requirements (2/2)

- ❑ Minimize the clock cycle by changing the delays in the module **mult_tb**
 - What is the minimum clock cycle?
 - Use tick as time unit
 - Show the waveform with the settings in **lab2.sav**
 - Should include 1750 to 1800 sec

Outline

- ❑ Multiplier
- ❑ Pipeline
- ❑ Fast Multiplier
- ❑ Assignment
- ❑ **Appendix**

Multiplier and Pipelining

- ❑ Signed multiplier

- <http://courses.csail.mit.edu/6.111/f2008/handouts/L09.pdf>

- ❑ Details on pipelining

- <https://www.slideshare.net/siddiqueibrahim37/pipelining-41608675>

- ❑ Details on fast multiplier

- <https://link.springer.com/article/10.1007/s11265-012-0657-7>

Some Details on Verilog

❑ Expression bit width

- http://yangchangwoo.com/podongii_X2/html/technote/TOOL/MANUAL/21i_doc/data/fndtn/ver/ver4_4.htm

❑ Event queue

- Determine the order of different types of assignment
- <http://www.ece.lsu.edu/v/2015/lsl-event-q.pdf>

❑ Transport delay and inertial delay

- http://www-inst.eecs.berkeley.edu/~cs152/fa06/handouts/CummingsHDLCON1999BehavioralDelays_Rev1_1.pdf

Q&A